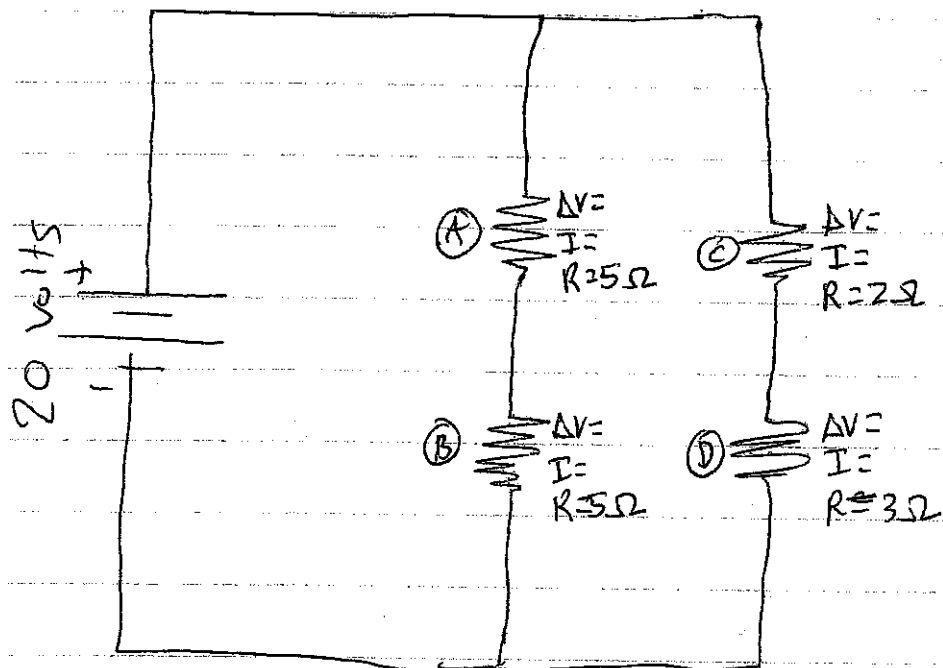


65

$$\Delta V = I \cdot R$$





Electric Potential (V)

20
10
0
-10
-20

5

- ① - Draw an equivalent circuit
- ② - Solve the equivalent circuit
- ③ - Draw the current on the equivalent circuit
- ④ - Go back to the original circuit and draw the current on it
- ⑤ - Solve each element of the original circuit

$$\Delta V = I \cdot R$$

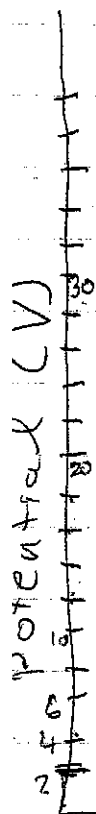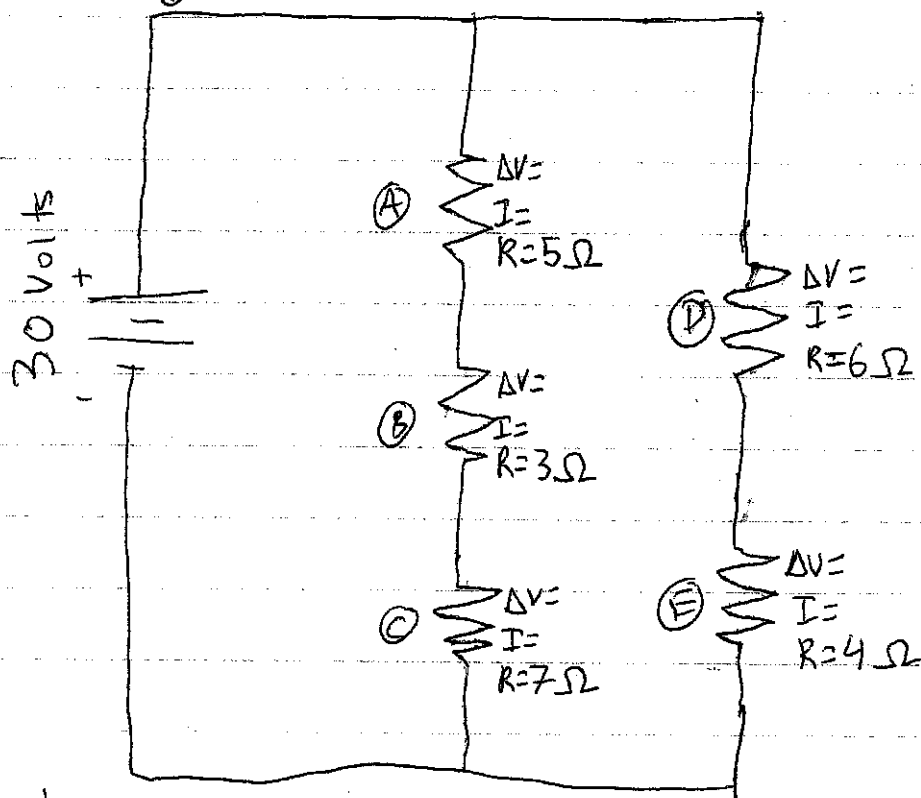


Different steps!

6.7

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

→ formula to add resistors in parallel

$$\Delta V = 36V$$

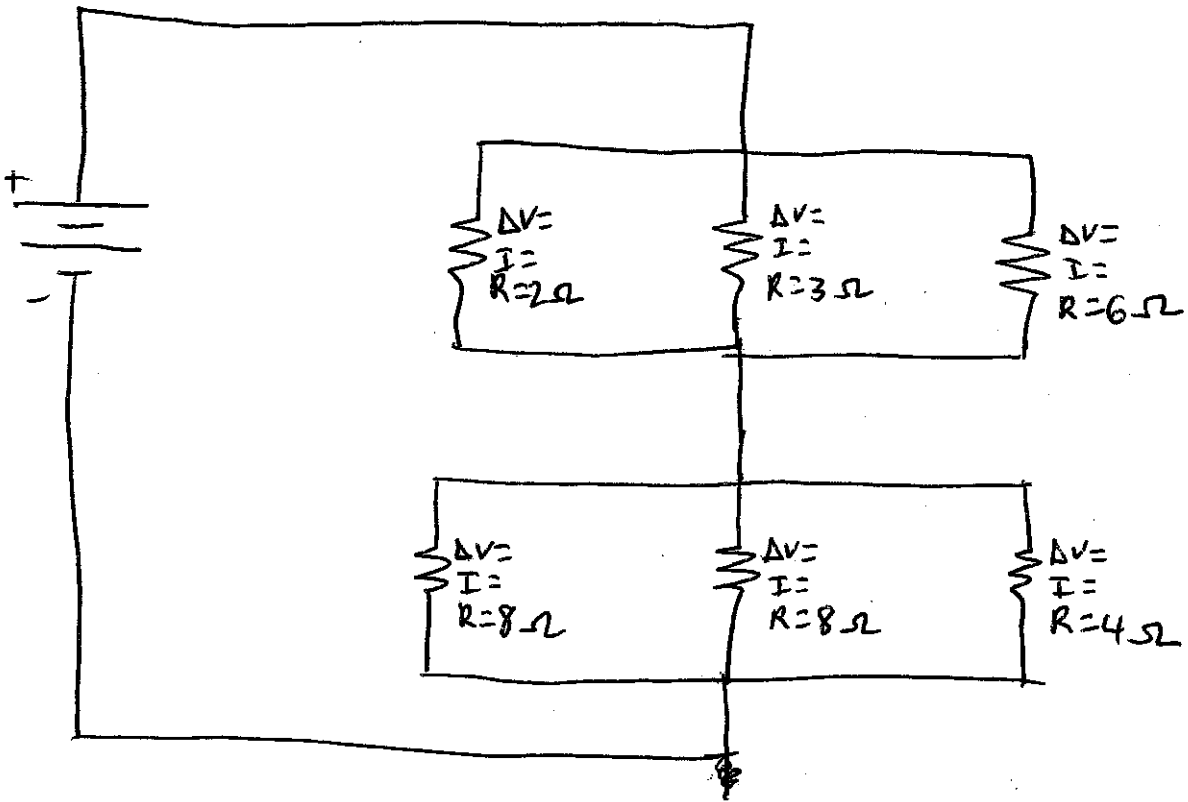

Draw the equivalent circuit here


G.7 cont.

electric potential (V)



36

24

12

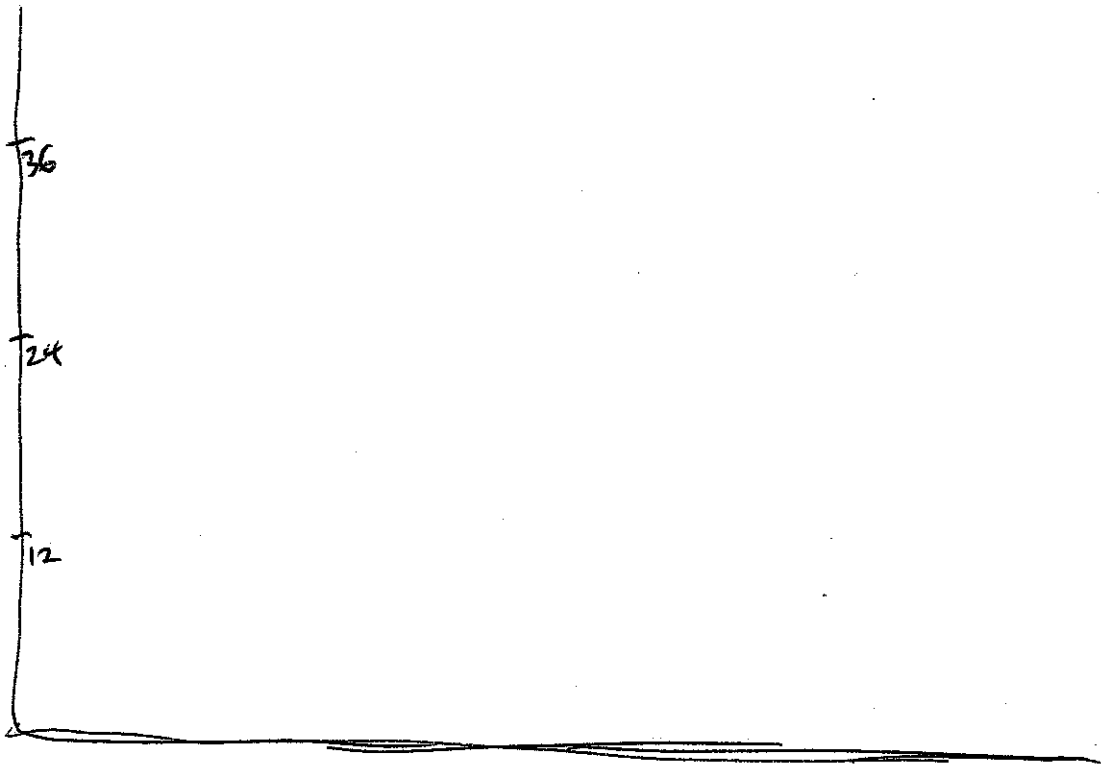

Electric Potential (V)

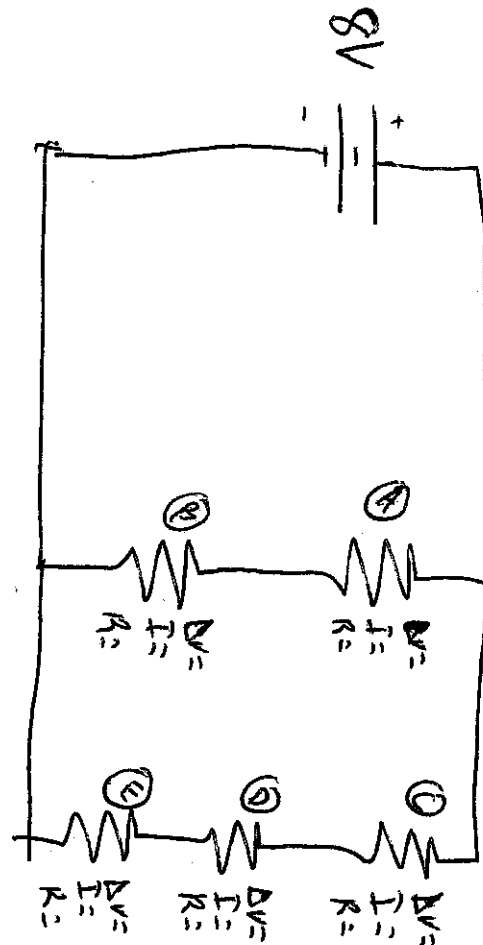
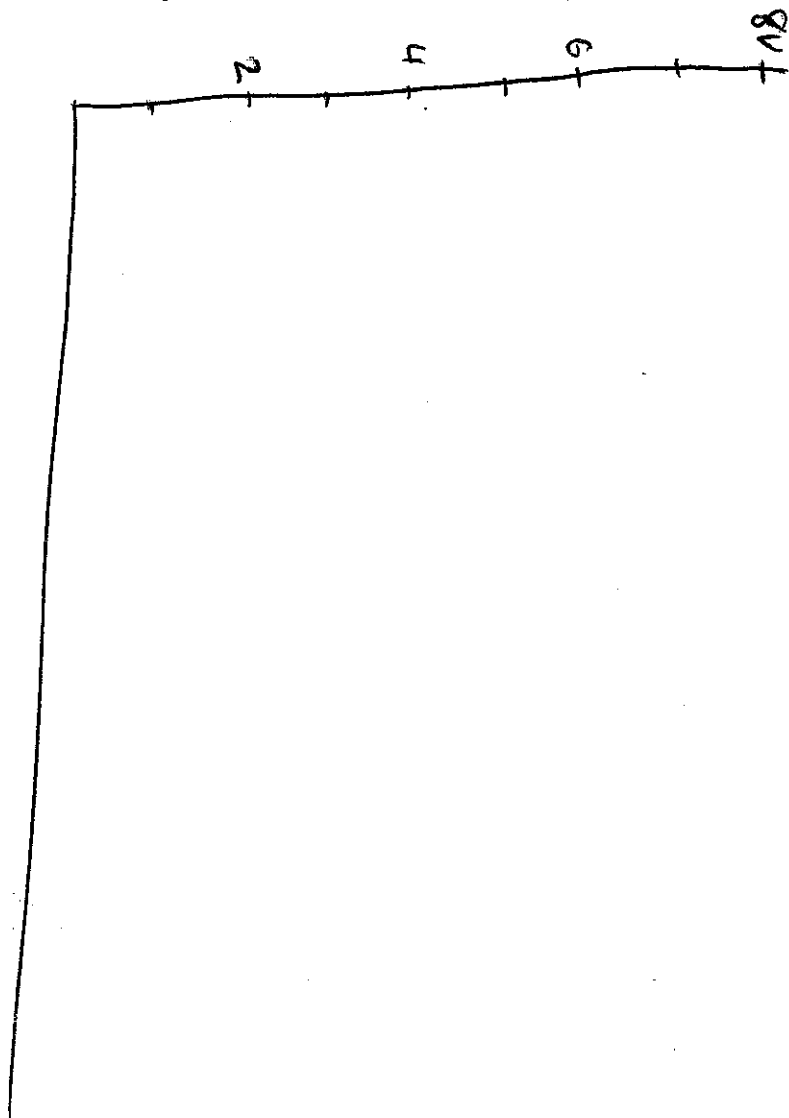


Equivalent Circuit

G.8'



(5.9)

Equivalent Circuit

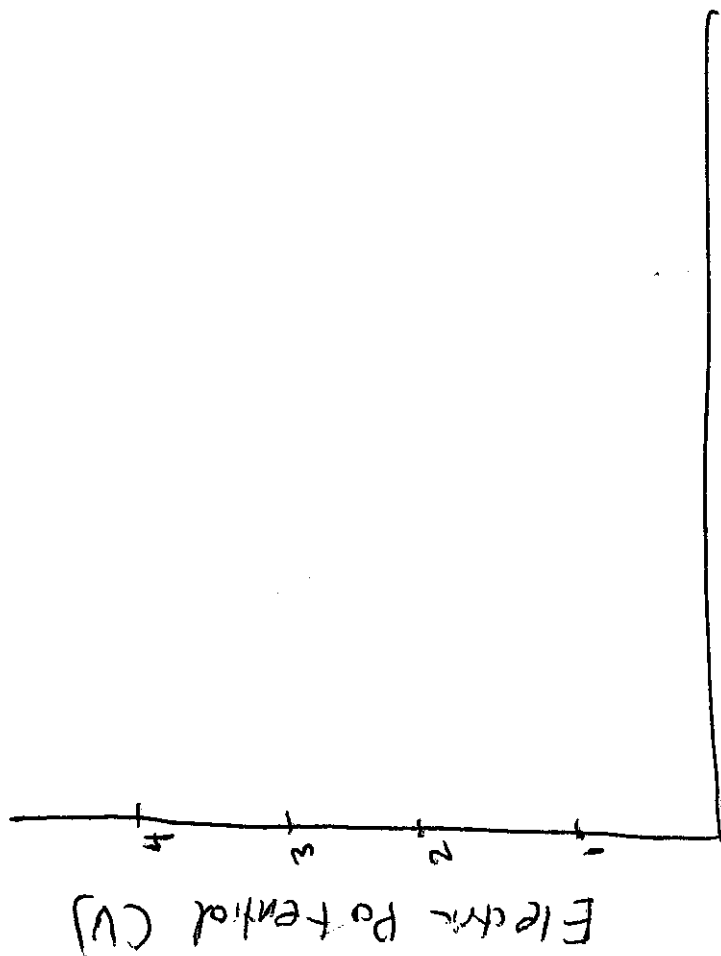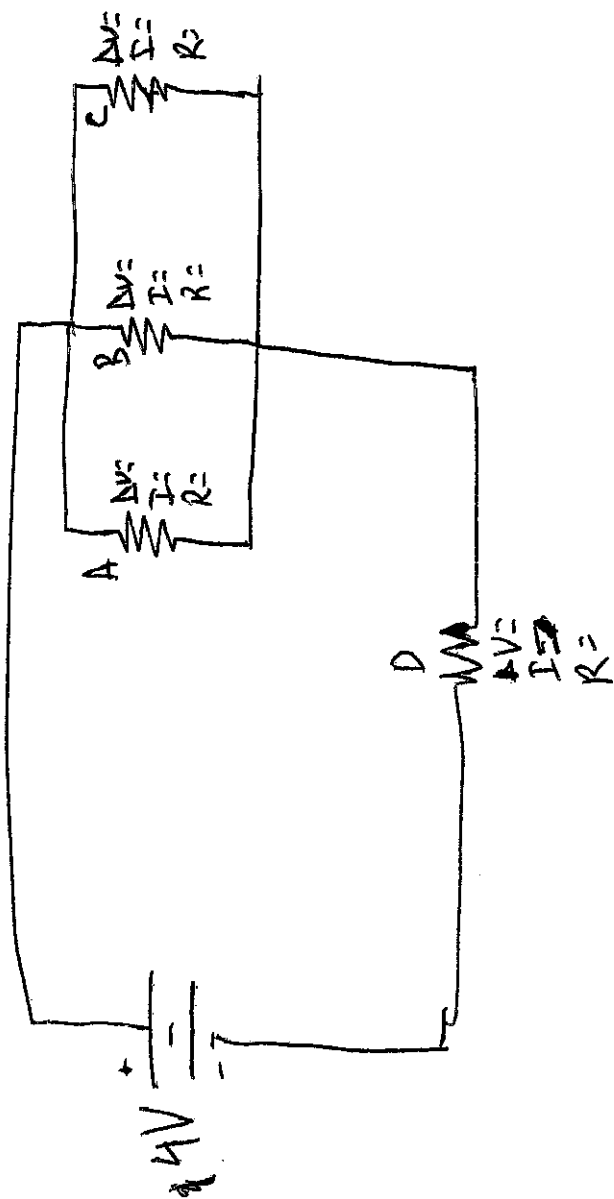

G.10

Drum Equivalent Circuit

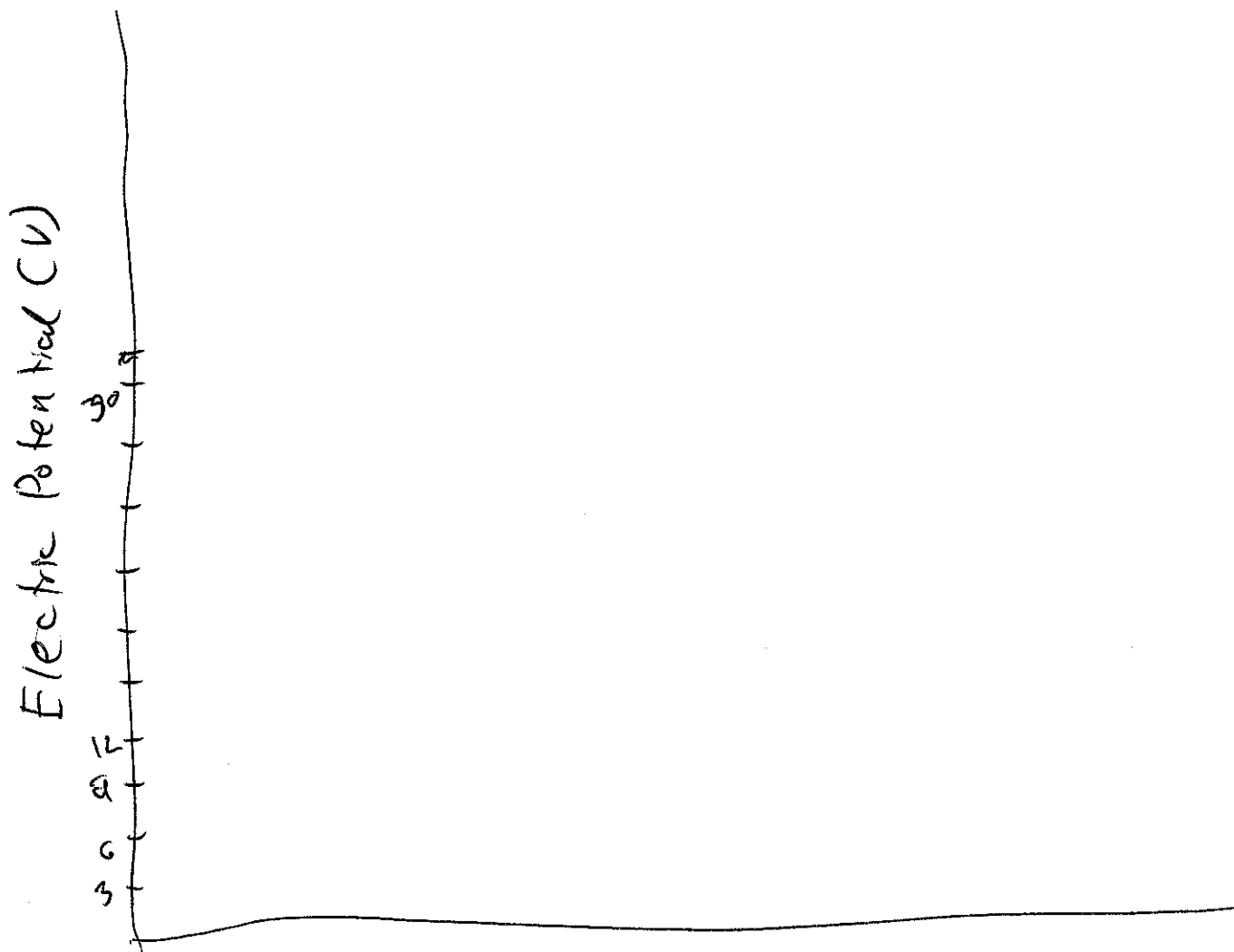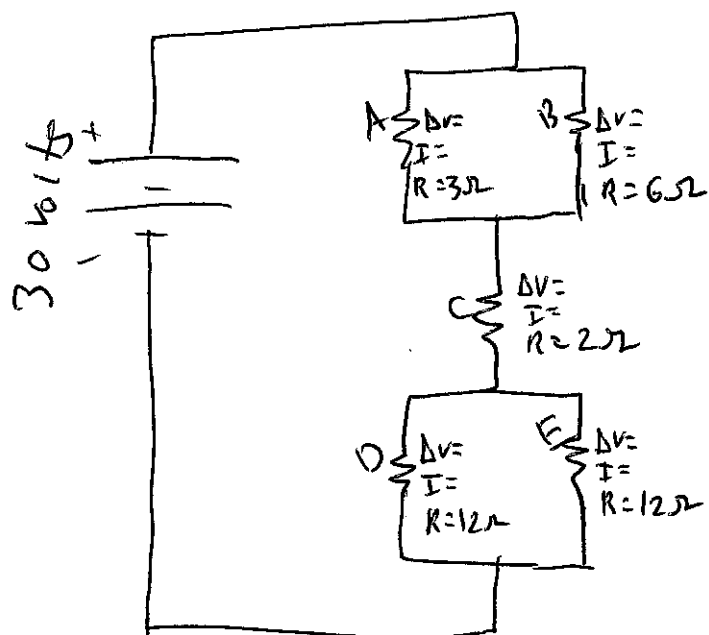

G.11

Draw an
Equivalent
Circuit

