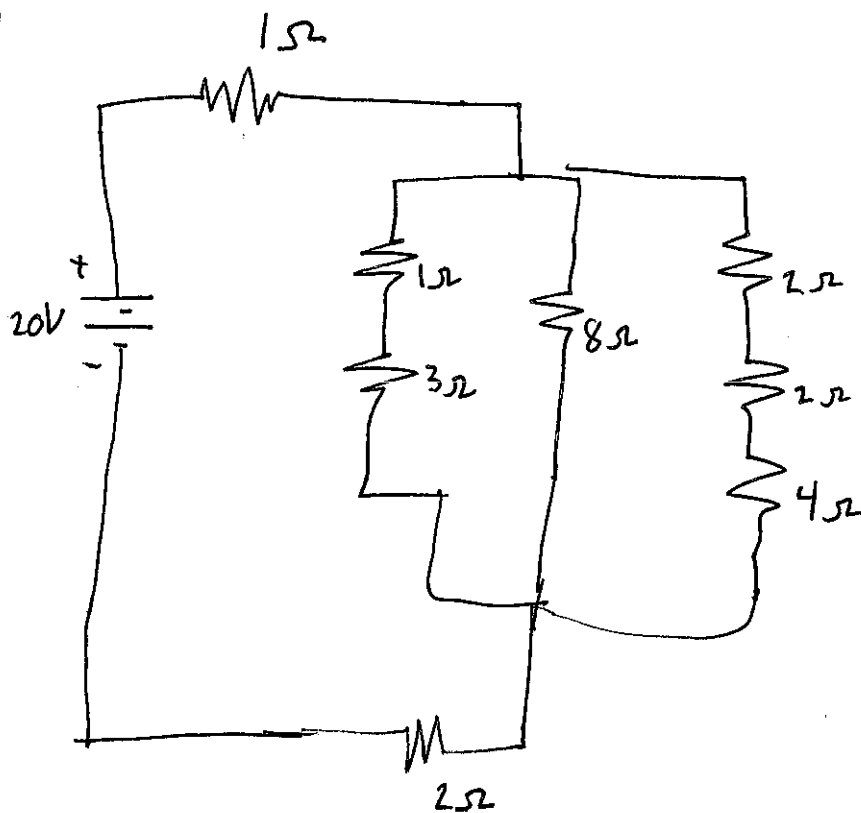


5 do on a separate page!




④ find the voltage, current,
resistance, and power of each resistor.

⑤ create a graph of electric potential ~~to~~
for the circuit.

Label the current on each branch of
your graph.

Label each resistor on your graph.

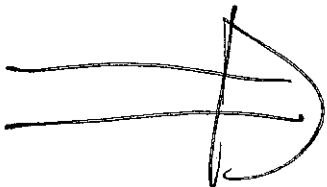ⓧ  back

- ② identify 2 junctions on your graph and prove they correctly follow the junction rule
- ③ identify 2 loops on your graph and prove that they correctly follow the loop rule
- ④ prove the circuit follows the conservation of energy by showing that the power ^{inputted} ~~emitted~~ by the battery is equal to the power outputted by ~~the~~ the resistors