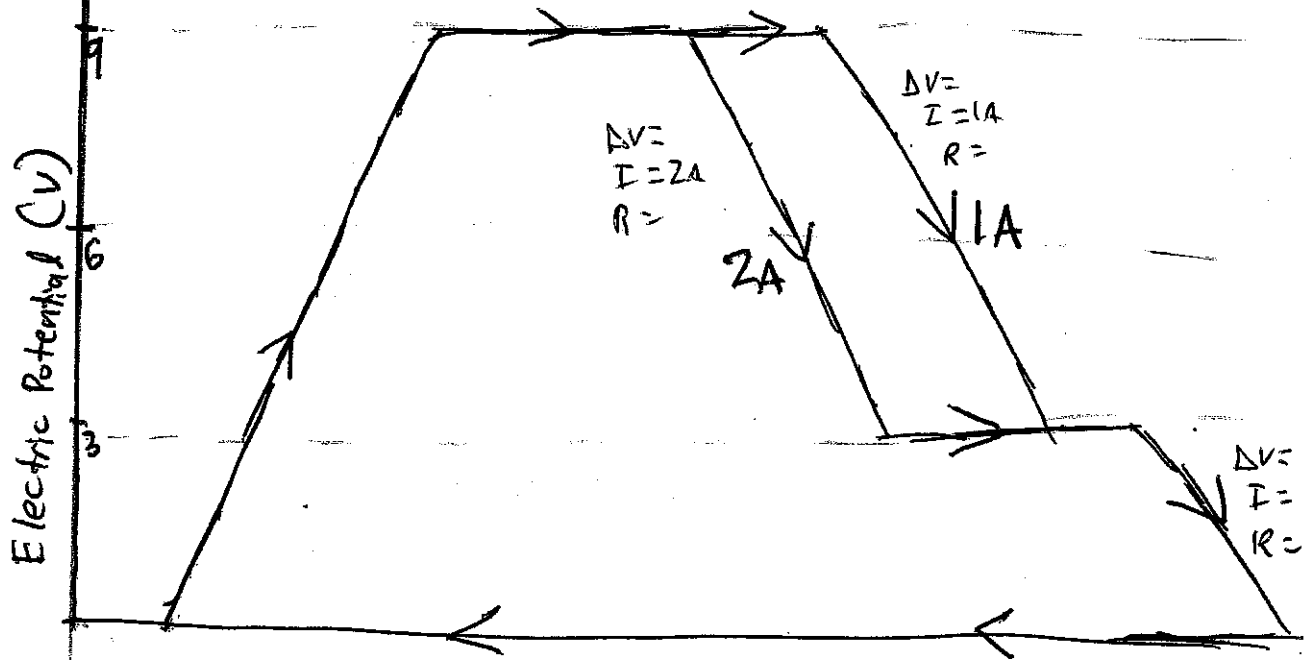


(H) 1




~~For the electric~~

Draw a circuit that could have the electric potential graph above.

For your final answer, draw the correct circuit with the voltage of the battery and the resistance of each resistor labeled. You do not need to make a table and solve the circuit, what you are doing here is going the other way, from the fully analyzed circuit to a picture of the real circuit!

H.2

Electric potential (V)

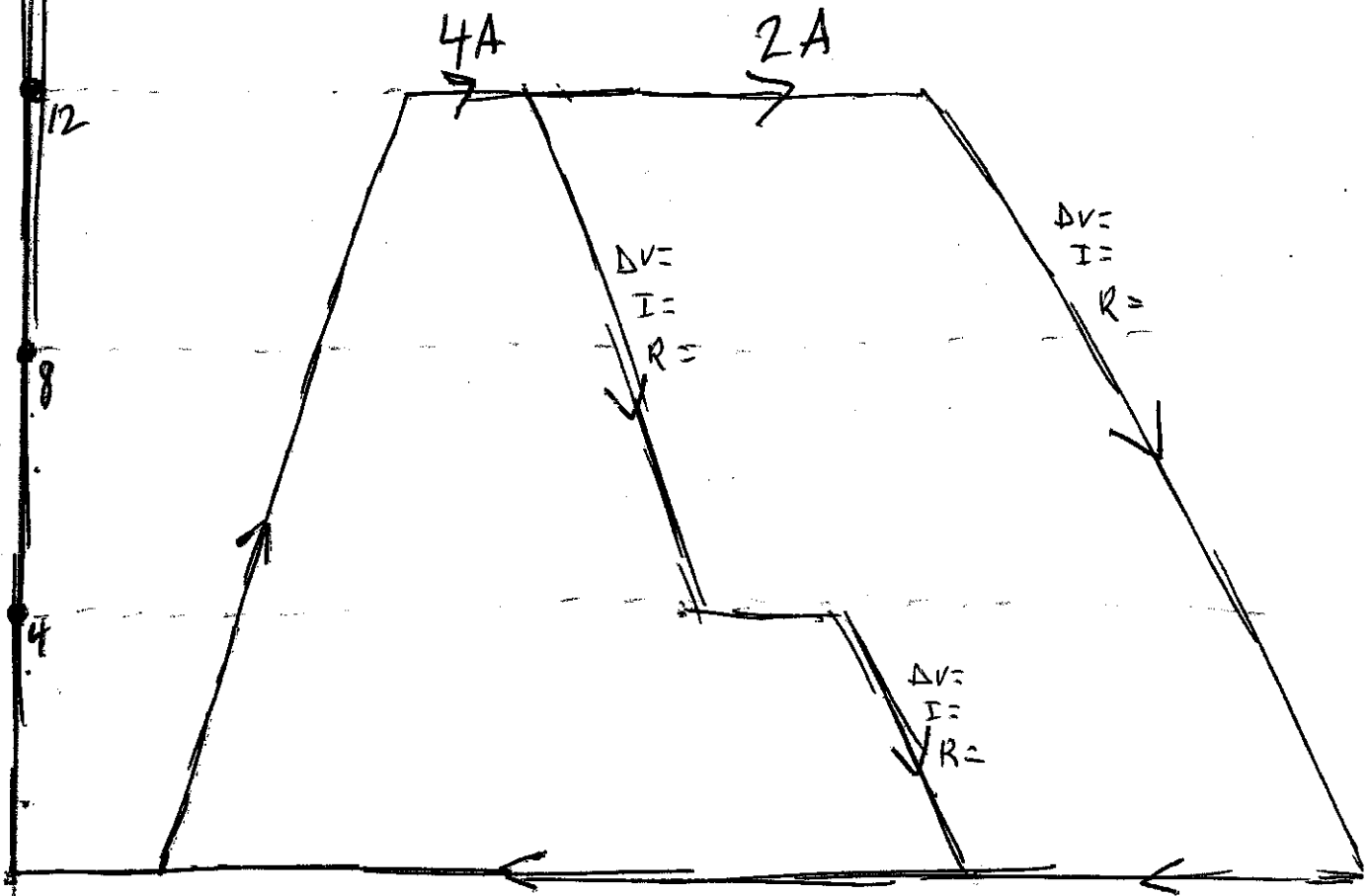


Draw a circuit that would have the electric potential graph pictured above

113


Directions:

Draw a circuit corresponding to this electric potential graph. Label the resistance of each resistor on the circuit.


electric potential (V)

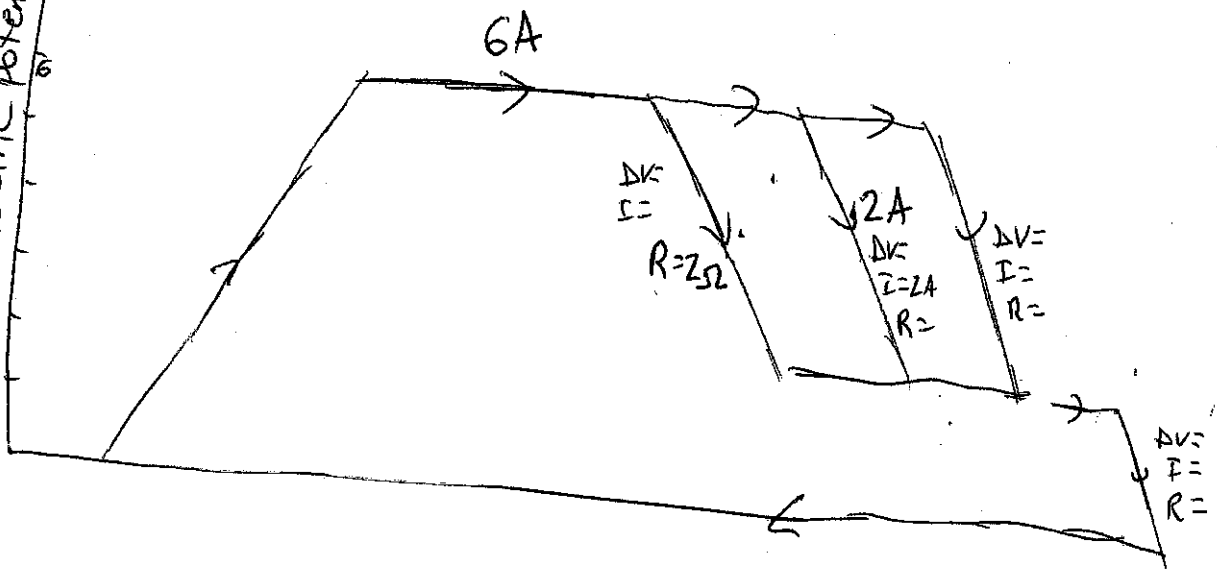


H. 24

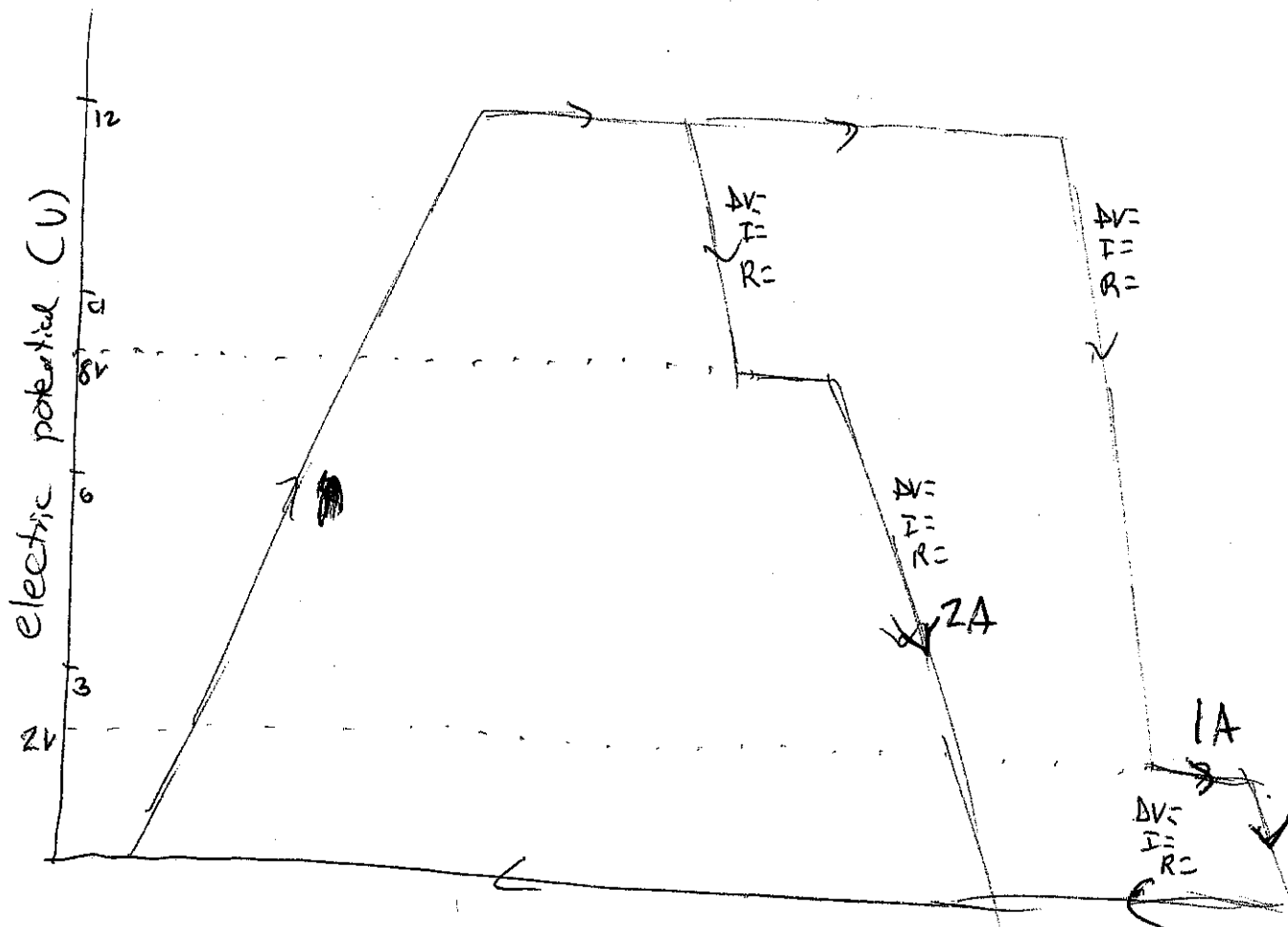

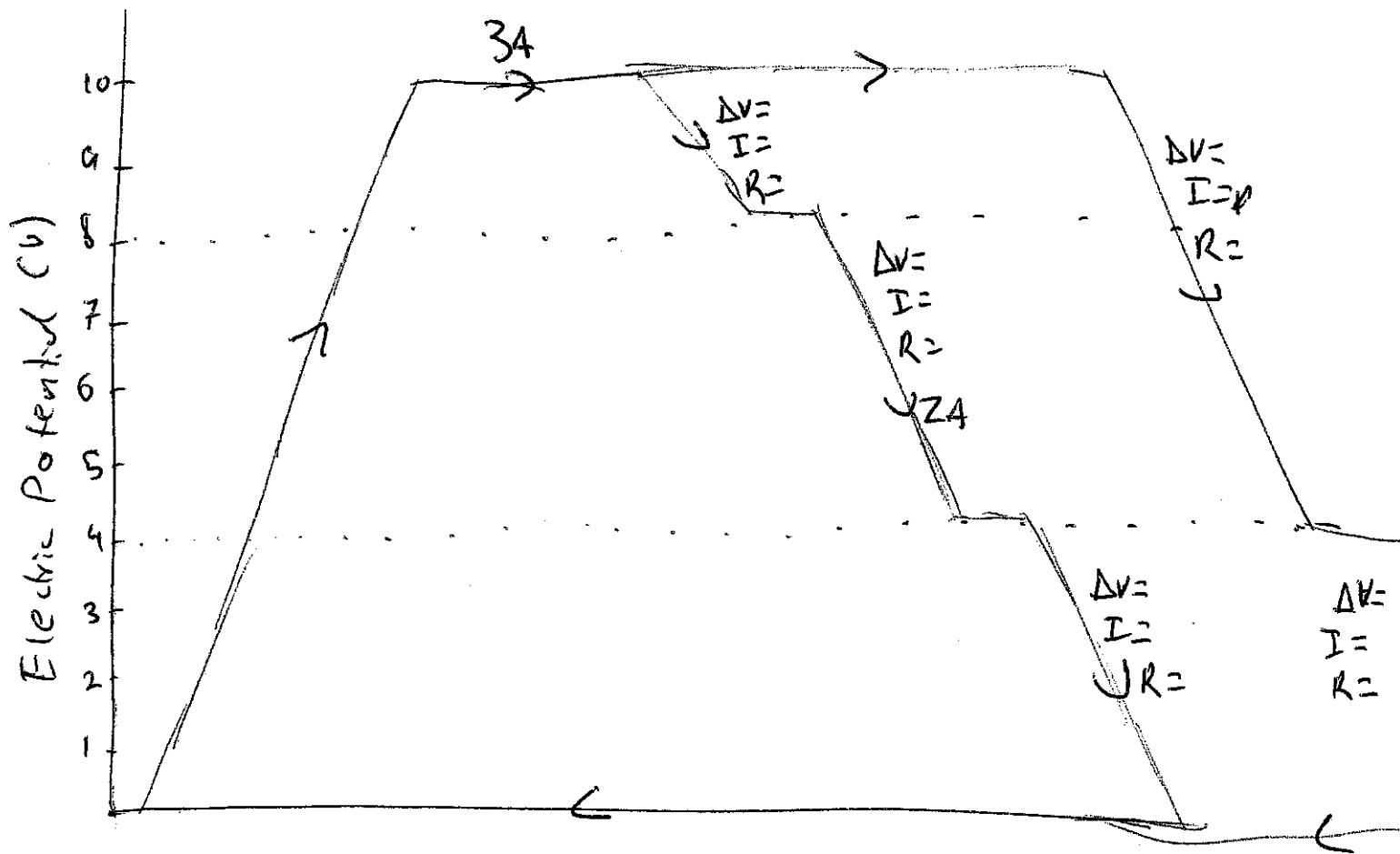Draw a circuit for this electric potential Graph




(H.6 2)

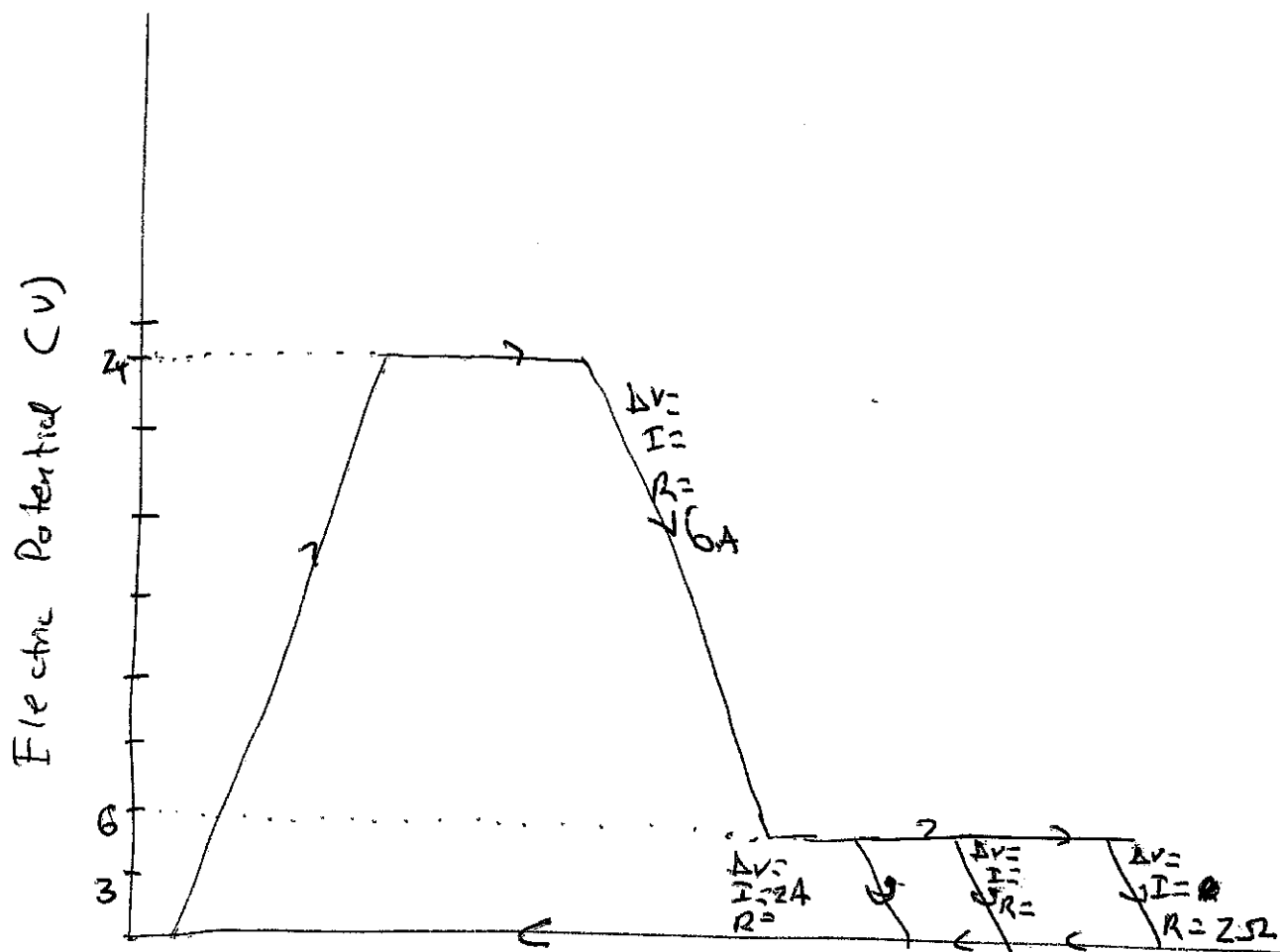

(H).1


Answer

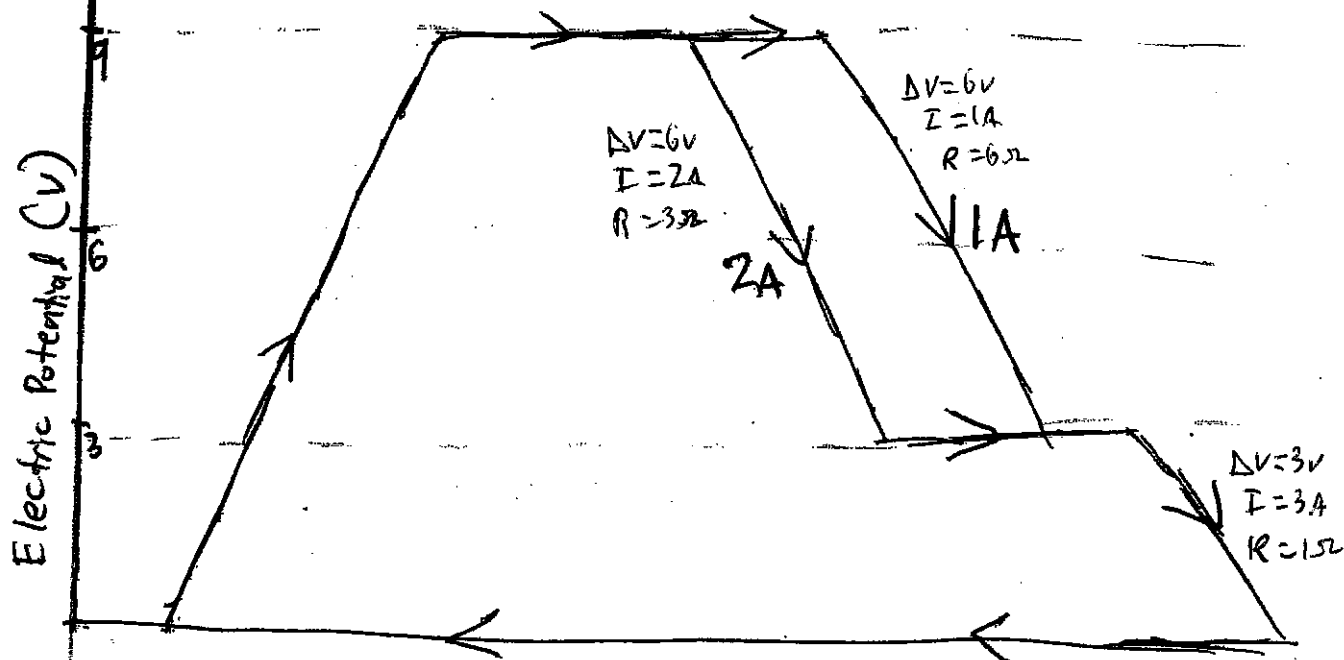


~~For your final answer, draw the correct circuit with the voltage of the battery and the resistance of each resistor labeled.~~

Draw a circuit that could have the electric potential graph above.

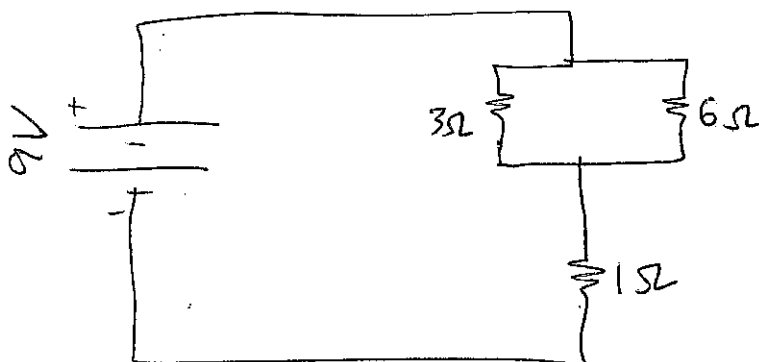
For your final answer, draw the correct circuit with the voltage of the battery and the resistance of each resistor labeled.
You do not need to make a table and solve the circuit, what you are doing here is going the other way, from the fully analyzed circuit to a picture of the real circuit!



H.2

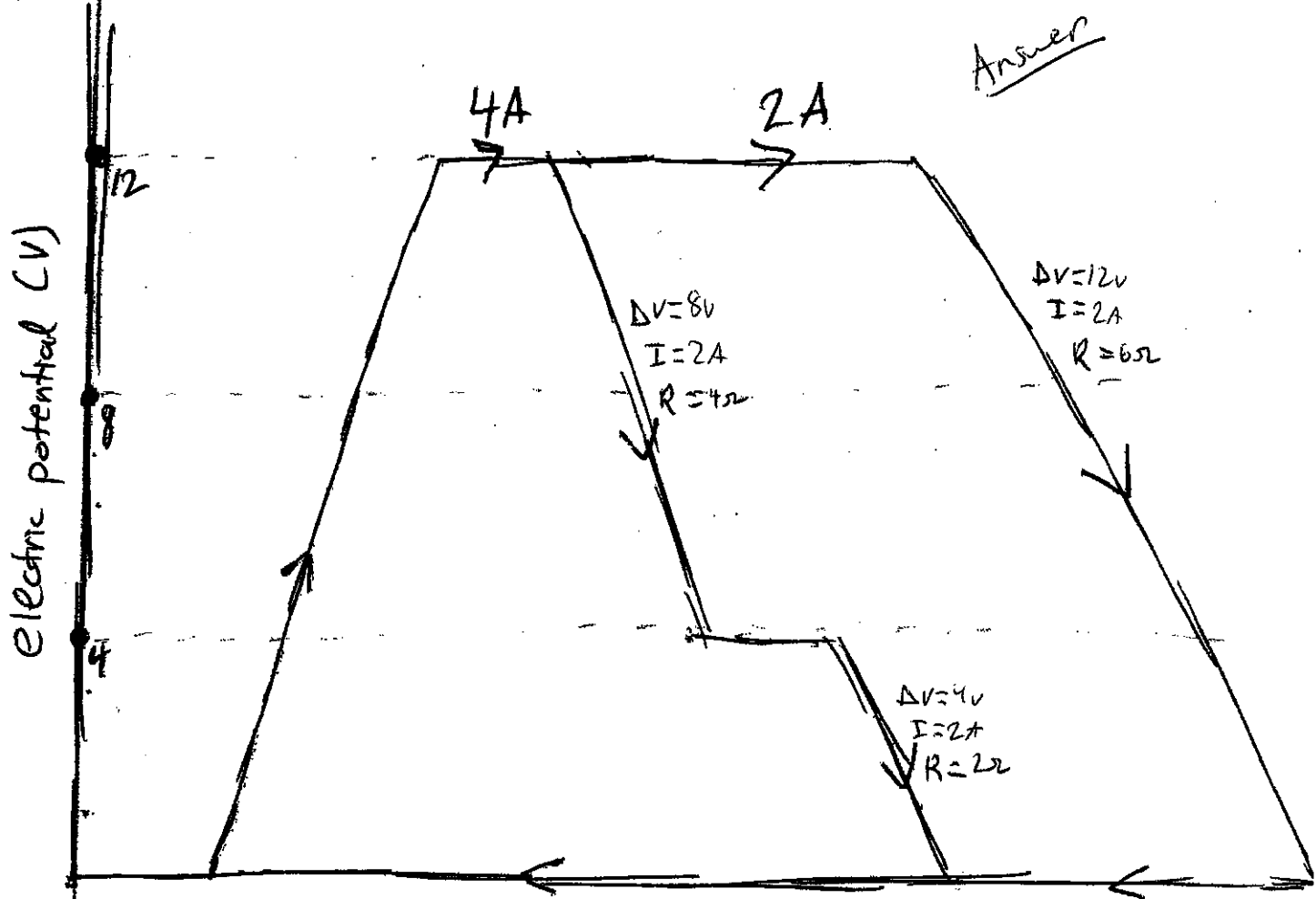


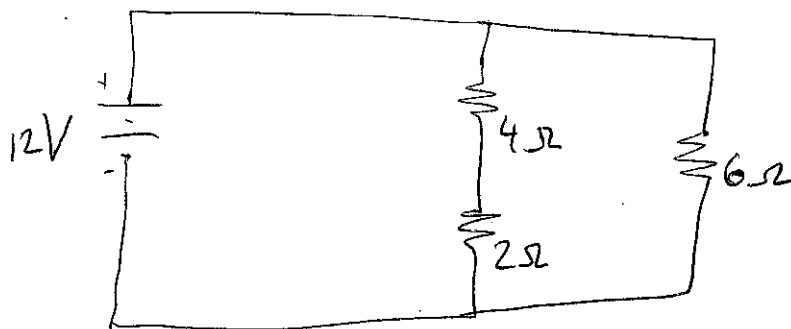
Draw a circuit that would have the electric potential graph pictured above



113

Directions:
 Draw a circuit corresponding
 to this electric potential graph.
 Label the resistance of each
 resistor on the circuit.

Answer

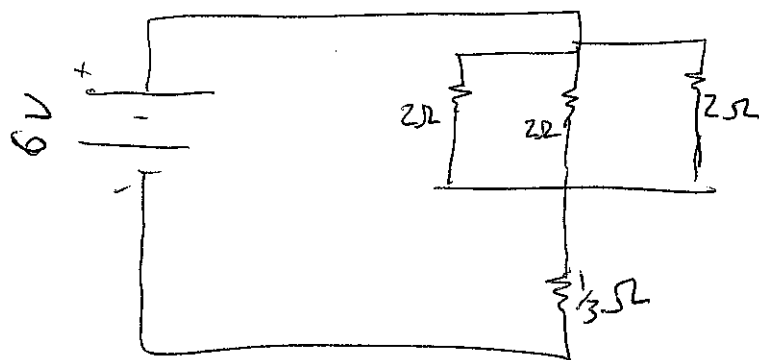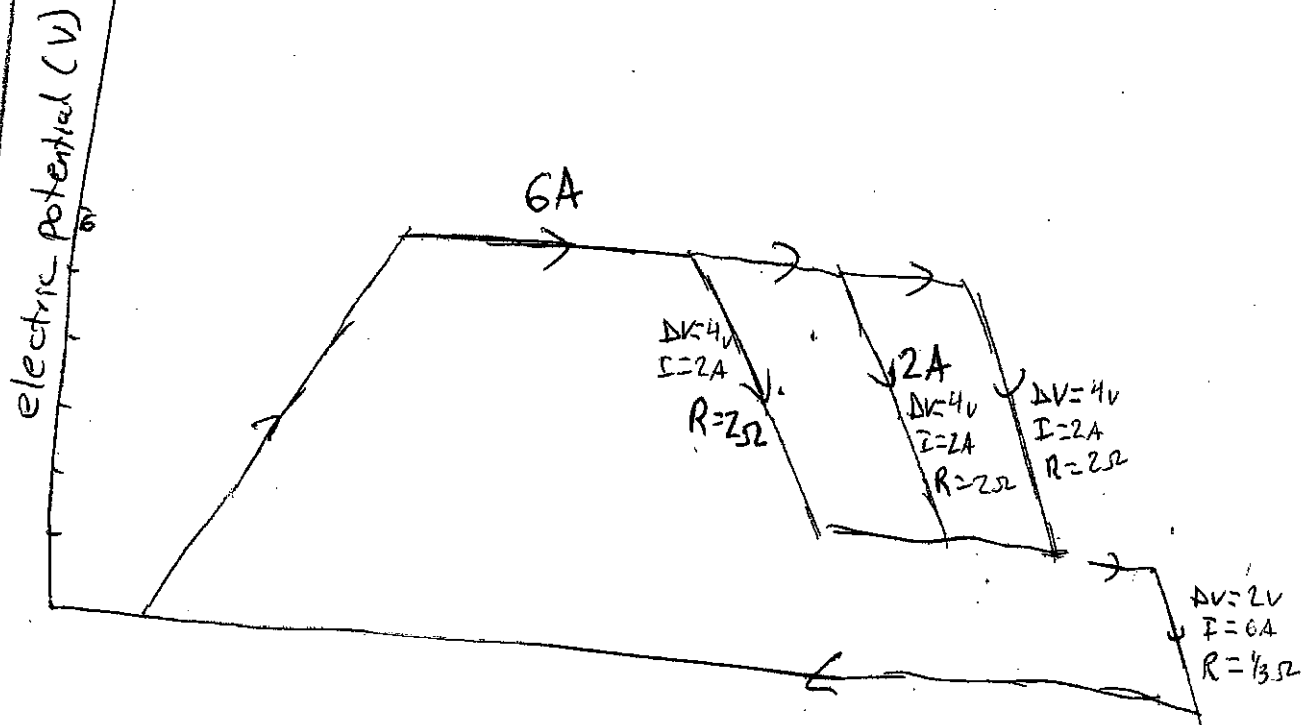

H. 24

Answer

