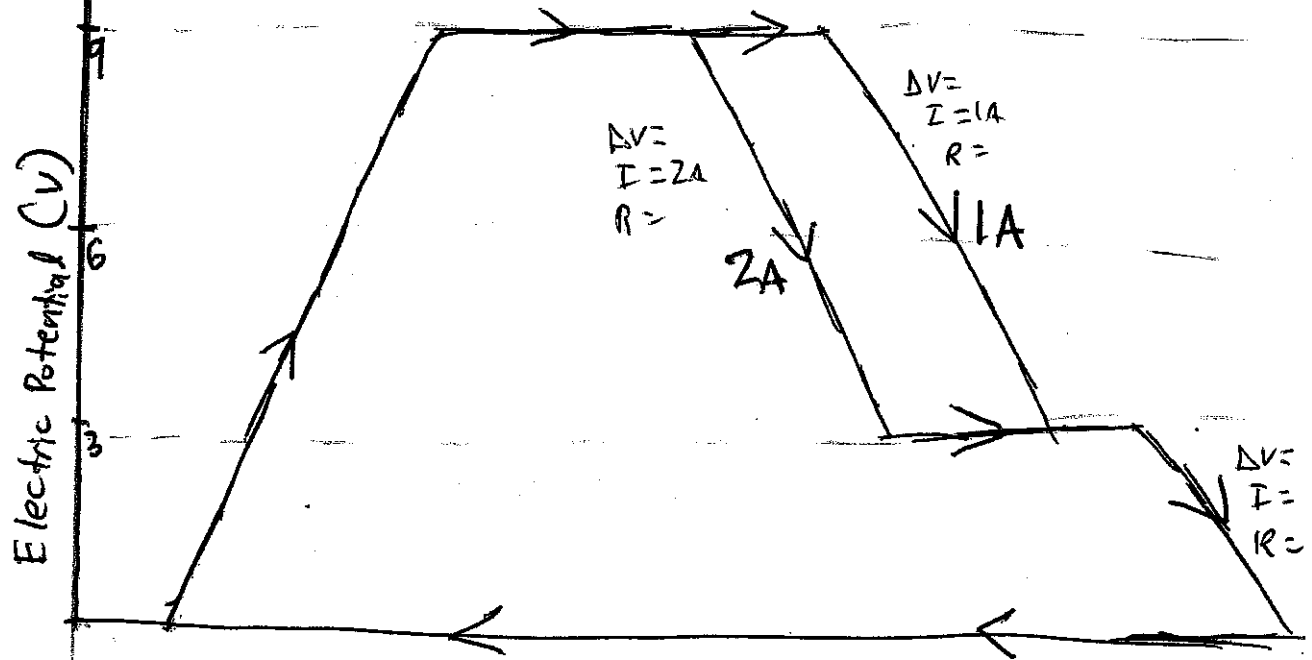


(H).1




~~For the electric~~

Draw a circuit that could ~~be~~  
have the electric potential graph above.

H.2

Electric potential (V)

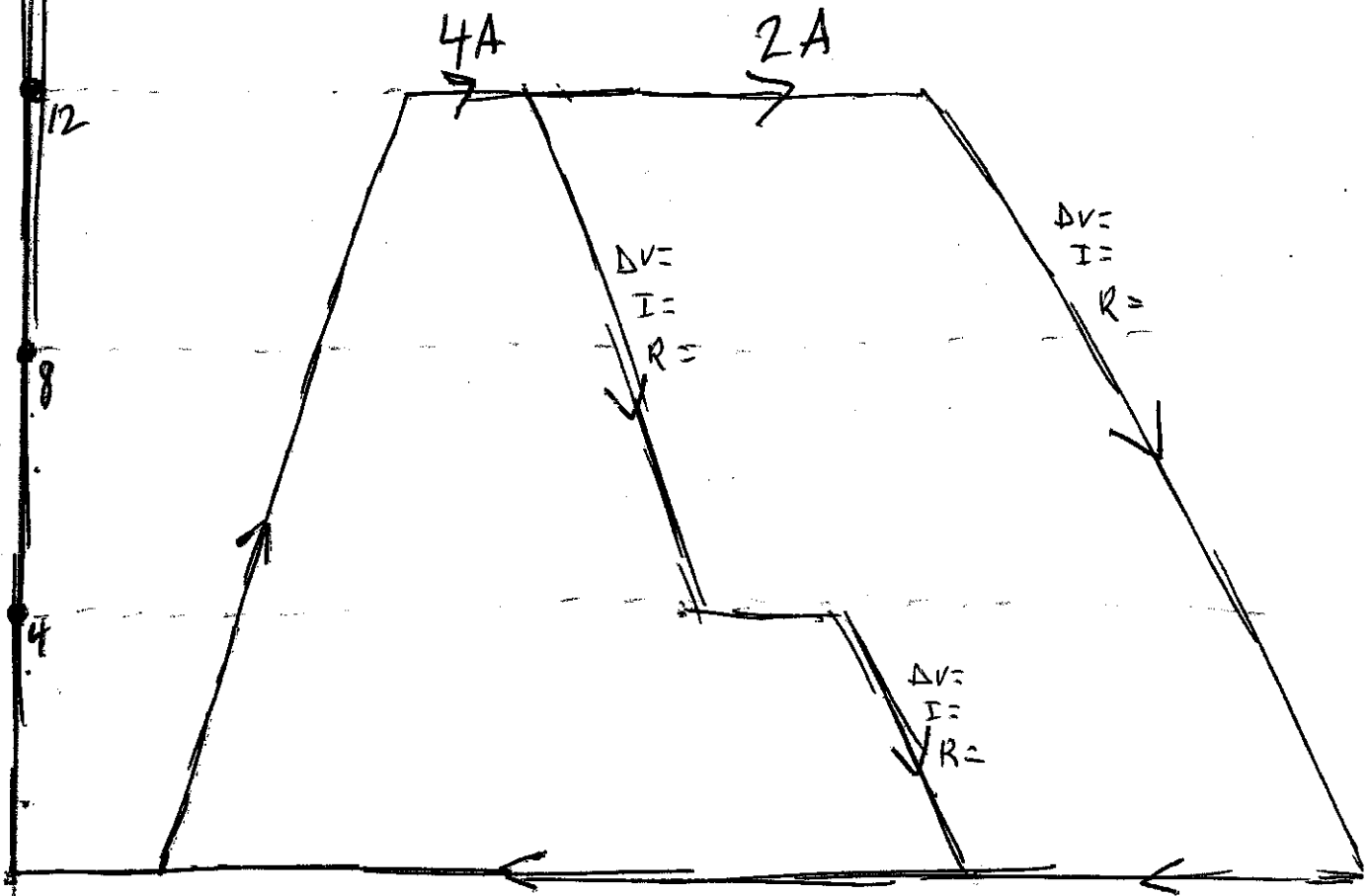


Draw a circuit that would have the electric potential graph pictured above

113

Directions:

Draw a circuit corresponding to this electric potential graph. Label the resistance of each resistor on the circuit.

electric potential (V)

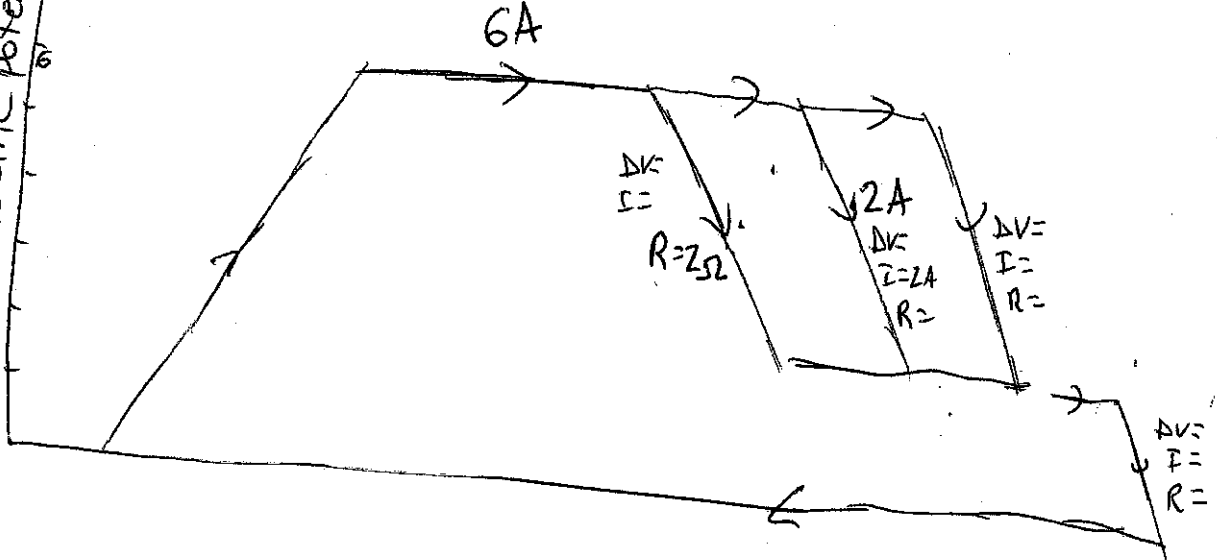

H. 24

