

**Part A: Ohm's Law**

$$V = IR$$

Symbol	Quantity	SI Unit	
V	Voltage	Volt (V)	
I	Current	Ampere (A)	
R	Resistance	Ohm ( $\Omega$ )	$\Omega$ is the Greek letter omega.

**A.1** What is the name of this letter:  $\Omega$  ? \_\_\_\_\_

What does it stand for in physics? \_\_\_\_\_

**A.2** What does "I" stand for? \_\_\_\_\_

**A.3** I hook up a circuit with a 10 V battery and a 5  $\Omega$  light bulb. What is the current?

Looking For	Formula	
Already Know		
Answer as a complete sentence <i>with unit</i> :		

**A.4** I hook up a circuit with a 30 V battery and a 6  $\Omega$  light bulb. What is the current?

Looking For	Formula	
Already Know		
Answer as a complete sentence <i>with unit</i> :		

**A.5** When I hook up a 12 V battery, I get 3 A of current. What is the resistance of my circuit?

Looking For	Formula	
Already Know		
Answer as a complete sentence <i>with unit</i> :		

Name \_\_\_\_\_

--

**A.6** I have 5 A of current going through a 10 Ohm resistor. What is the voltage of my circuit?

Looking For	Formula	
Already Know		
Answer as equation <i>with unit</i> :		

**A.7** I have 3 A of current going through a 5 Ohm resistor. What is the voltage of my circuit?

Looking For	Formula	
Already Know		
Answer as a complete sentence <i>with unit</i> :		

**A.8** I hook up a 12 V battery to a 36  $\Omega$  resistor. What is the current in my circuit?

Looking For	Formula	
Already Know		
Answer as a complete sentence <i>with unit</i> :		

**Part B: Ohm's Law table**

Each row of the following table contains two numbers given and one number still unknown. Fill in the unknown number so that each row satisfies the equation  $V = IR$ .

<b>Voltage (Volts)</b>	<b>Current (Amps)</b>	<b>Resistance (Ohms)</b>
24		4
15	5	
24		12
20	4	
	2	9
	3	12
10		20

**Answers:**

**A.1** omega; it stands for Ohms

**A.2** current

**A.3** 2 Amps

**A.4** 5 Amps

**A.5** 4 Ohms

**A.6** 50 Volts

**A.7** 15 Volts

**A.8** 0.33 Amps