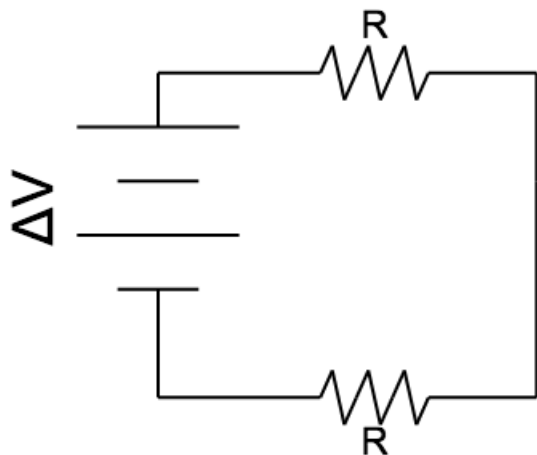


Part I: Solving Full Circuits Algebraically

When solving a full circuit algebraically, you can follow the same set of rules that would be followed for solving a circuit with numerical values!

I.1 You have a **series** circuit with a battery and two **identical** resistors. The potential difference across the battery is ΔV and the resistance of each resistor is R



a) Determine all relevant quantities for this circuit algebraically in terms of ΔV and R by filling in the following table.


	Resistor A	Resistor B	Total (Battery)
Potential Difference			
Current			
Resistance			
Power			

b) Confirm that your answer follows the *conservation of energy*. That is, the power of each resistor adds to the total power:

$$P_A + P_B = P_{tot} = \Delta V \cdot I_{tot}$$

Part I: Solving Full Circuits Algebraically

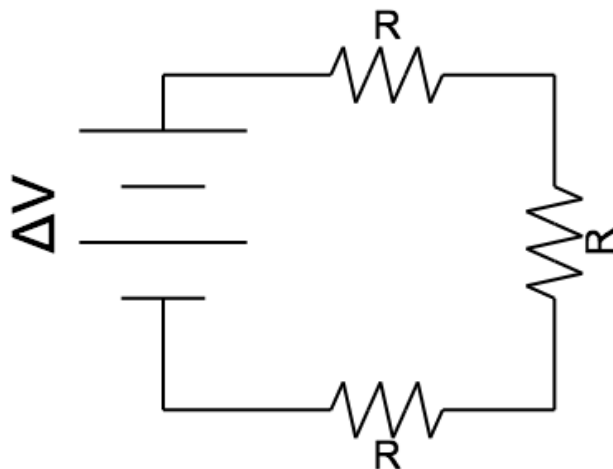I.2 You have a **series** circuit with a battery and *three identical* resistors. The potential difference across the battery is ΔV and the resistance of each resistor is R .



a) Determine all relevant quantities for this circuit algebraically in terms of ΔV and R by filling in the following table.


	Resistor A	Resistor B	Resistor C	Total (Battery)
Potential Difference				
Current				
Resistance				
Power				

b) Confirm that your answer follows the *conservation of energy*. That is, the power of each resistor adds to the total power:

$$P_A + P_B + P_C = P_{tot} = \Delta V \cdot I_{tot}$$

Part I: Solving Full Circuits Algebraically

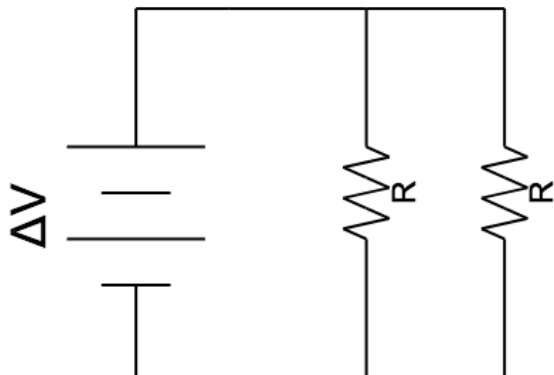I.3 You have a **parallel** circuit with a battery and two **identical** resistors. The potential difference across the battery is ΔV and the resistance of each resistor is R . Determine all relevant quantities for this circuit algebraically by filling in the following table.



a) Determine all relevant quantities for this circuit algebraically in terms of ΔV and R by filling in the following table.


	Resistor A	Resistor B	Total (Battery)
Potential Difference			
Current			
Resistance			
Power			

b) Confirm that your answer follows the *conservation of energy*. That is, the power of each resistor adds to the total power:

$$P_A + P_B = P_{tot} = \Delta V \cdot I_{tot}$$

Part I: Solving Full Circuits Algebraically

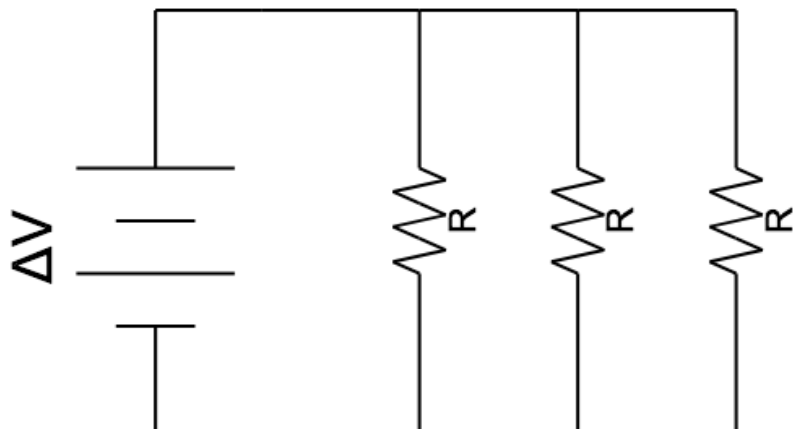I.4 You have a **parallel** circuit with a battery and *three identical* resistors. The potential difference across the battery is ΔV and the resistance of each resistor is R . Determine all relevant quantities for this circuit algebraically by filling in the following table.



a) Determine all relevant quantities for this circuit algebraically in terms of ΔV and R by filling in the following table.

	Resistor A	Resistor B	Resistor C	Total (Battery)
Potential Difference				
Current				
Resistance				
Power				


b) Confirm that your answer follows the *conservation of energy*. That is, the power of each resistor adds to the total power:

$$P_A + P_B + P_C = P_{tot} = \Delta V \cdot I_{tot}$$

Part I: Solving Full Circuits Algebraically

I.5

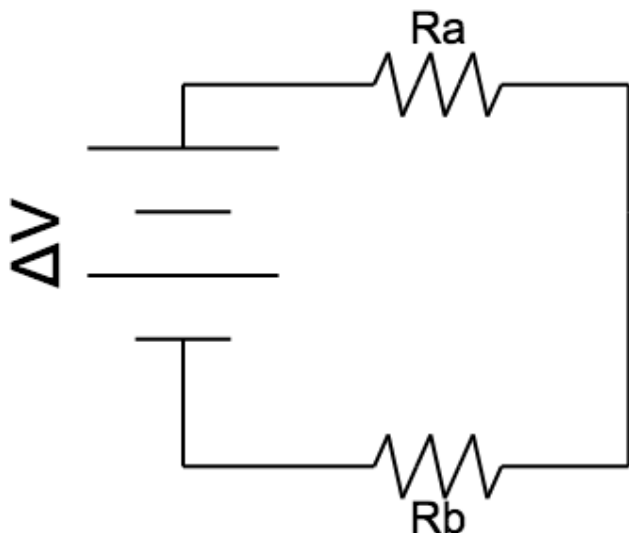You have a **series** circuit with a battery and two resistors. **The two resistors are not identical**, they now have resistances of R_a and R_b , where $R_a \neq R_b$. The potential difference across the battery is ΔV .



a) Determine all relevant quantities for this circuit algebraically in terms of ΔV , R_a , and R_b by filling in the following table.

	Resistor A	Resistor B	Total (Battery)
Potential Difference			
Current			
Resistance			
Power			


b) Confirm that your answer follows the *conservation of energy*. That is, the power of each resistor adds to the total power:

$$P_A + P_B = P_{tot} = \Delta V \cdot I_{tot}$$

Part I: Solving Full Circuits Algebraically

I.6

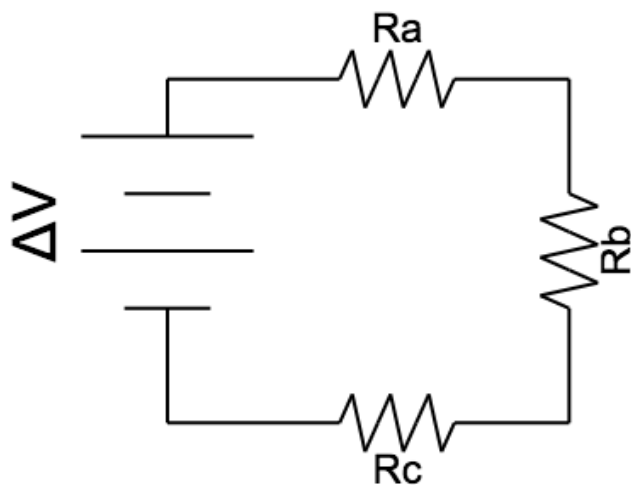You have a **series** circuit with a battery and three resistors. **The three resistors are not identical**, they now have resistances of R_a , R_b and R_c , where $R_a \neq R_b \neq R_c$. The potential difference across the battery is ΔV .



a) Determine all relevant quantities for this circuit algebraically in terms of ΔV , R_a , R_b , and R_c by filling in the following table.

	Resistor A	Resistor B	Resistor C	Total (Battery)
Potential Difference				
Current				
Resistance				
Power				


b) Confirm that your answer follows the *conservation of energy*. That is, the power of each resistor adds to the total power:

$$P_A + P_B = P_{tot} = \Delta V \cdot I_{tot}$$

Part I: Solving Full Circuits Algebraically

I.7

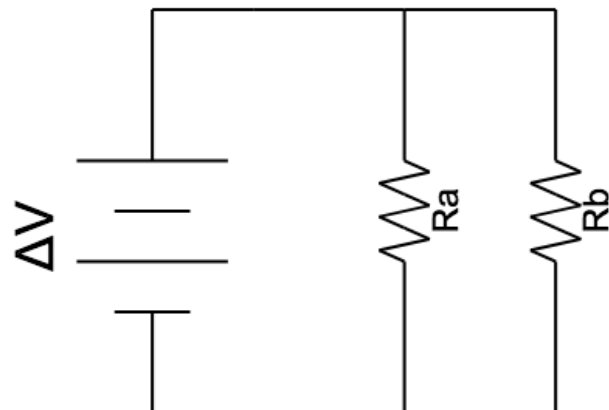You have a **parallel** circuit with a battery and two resistors. **The two resistors are not identical**, they now have resistances of R_a and R_b , where $R_a \neq R_b$. The potential difference across the battery is ΔV .



a) Determine all relevant quantities for this circuit algebraically in terms of ΔV , R_a , and R_b by filling in the following table.

	Resistor A	Resistor B	Total (Battery)
Potential Difference			
Current			
Resistance			
Power			

Part I: Solving Full Circuits Algebraically

b) Confirm that your answer follows the *conservation of energy*. That is, the power of each resistor adds to the total power:

$$P_A + P_B + P_C = P_{tot} = \Delta V \cdot I_{tot}$$

c) Problem **I.7** is actually the *derivation* of the formula for equivalent resistance of two resistors in parallel, which is always included in physics textbooks and used to solve combined circuits with two resistors in parallel:


$$\frac{1}{R_{tot}} = \frac{1}{R_A} + \frac{1}{R_B}$$

Show that your solution for *total resistance* matches this form.

Part I: Solving Full Circuits Algebraically

I.8

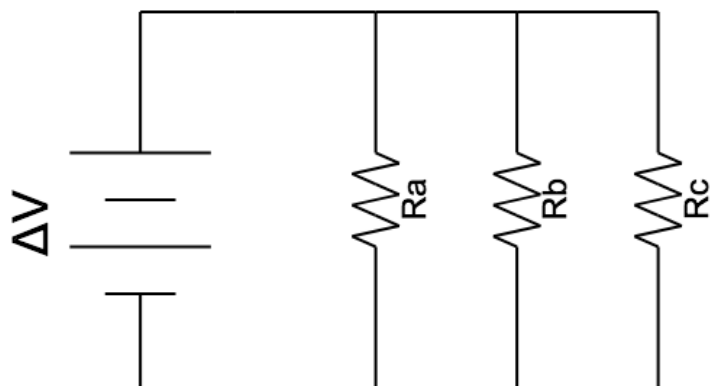You have a **parallel** circuit with a battery and three resistors. **The three resistors are not identical**, they now have resistances of R_a , R_b and R_c , where $R_a \neq R_b \neq R_c$. The potential difference across the battery is ΔV .



a) Determine all relevant quantities for this circuit algebraically in terms of ΔV , R_a , R_b , and R_c by filling in the following table.

	Resistor A	Resistor B	Resistor C	Total (Battery)
Potential Difference				
Current				
Resistance				
Power				

Part I: Solving Full Circuits Algebraically

b) Confirm that your answer follows the *conservation of energy*. That is, the power of each resistor adds to the total power:

$$P_A + P_B + P_C = P_{tot} = \Delta V \cdot I_{tot}$$

c) Problem **I.8** is actually the *derivation* of the formula for equivalent resistance of two resistors in parallel, which is always included in physics textbooks and used to solve combined circuits with two resistors in parallel:

$$\frac{1}{R_{tot}} = \frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C}$$

Show that your solution for *total resistance* matches this form.

Part I: Solving Full Circuits Algebraically

I.9

You have a series circuit with three identical resistors.

The potential difference of the battery is ΔV , and the total current of the circuit is I .

Solve for each relevant element of the circuit in terms of ΔV and I (*not* in terms of the resistance!)

I.10

You have a series circuit with n identical resistors.

The potential difference of the battery is ΔV , the total current of the circuit is I , and each resistor has resistance R .

Derive an equation for I in terms of ΔV , n , and R .

I.11

You have a parallel circuit with three identical resistors.

The potential difference of the battery is ΔV , and the total current of the circuit is I_{tot} .

Solve for each relevant element of the circuit in terms of ΔV and I (*not* in terms of the resistance!)

I.12

You have a parallel circuit with n identical resistors.

The potential difference of the battery is ΔV , the total current of the circuit is I_{tot} , and each resistor has resistance R .

Derive an equation for I_{tot} in terms of ΔV , n , and R .

I.13

You have a parallel circuit with n identical resistors, each of resistance R .

Derive an equation for the total resistance of the circuit in terms of R and n .

Part I: Solving Full Circuits Algebraically

I.1 ANSWER

a)

	Resistor A	Resistor B	Total (Battery)
Potential Difference	$\frac{\Delta V}{2}$	$\frac{\Delta V}{2}$	ΔV
Current	$\frac{\Delta V}{2R}$	$\frac{\Delta V}{2R}$	$\frac{\Delta V}{2R}$
Resistance	R	R	$2R$
Power	$\frac{(\Delta V)^2}{4R}$	$\frac{(\Delta V)^2}{4R}$	$\frac{(\Delta V)^2}{2R}$

b)

Confirm that the power of each resistor adds to the total power:

$$P_A + P_B = P_{tot} = \Delta V \cdot I_{tot}$$

$$\frac{(\Delta V)^2}{4R} + \frac{(\Delta V)^2}{4R} = \frac{(\Delta V)^2}{2R} = \frac{\Delta V}{1} \cdot \frac{\Delta V}{2R}$$

Part I: Solving Full Circuits Algebraically

I.2 ANSWER

a)

	Resistor A	Resistor B	Resistor C	Total (Battery)
Potential Difference	$\frac{\Delta V}{3}$	$\frac{\Delta V}{3}$	$\frac{\Delta V}{3}$	ΔV
Current	$\frac{\Delta V}{3R}$	$\frac{\Delta V}{3R}$	$\frac{\Delta V}{3R}$	$\frac{\Delta V}{3R}$
Resistance	R	R	R	$3R$
Power	$\frac{(\Delta V)^2}{9R}$	$\frac{(\Delta V)^2}{9R}$	$\frac{(\Delta V)^2}{9R}$	$\frac{(\Delta V)^2}{3R}$

b)

Confirm that the power of each resistor adds to the total power:

$$P_A + P_B + P_C = P_{tot} = \Delta V \cdot I_{tot}$$
$$\frac{(\Delta V)^2}{9R} + \frac{(\Delta V)^2}{9R} + \frac{(\Delta V)^2}{9R} = \frac{(\Delta V)^2}{3R} = \frac{\Delta V}{1} \cdot \frac{\Delta V}{3R}$$

Part I: Solving Full Circuits Algebraically

I.3 ANSWER

a)

	Resistor A	Resistor B	Total (Battery)
Potential Difference	ΔV	ΔV	ΔV
Current	$\frac{\Delta V}{R}$	$\frac{\Delta V}{R}$	$\frac{2(\Delta V)}{R}$
Resistance	R	R	$\frac{R}{2}$
Power	$\frac{(\Delta V)^2}{R}$	$\frac{(\Delta V)^2}{R}$	$\frac{2(\Delta V)^2}{R}$

b)

Confirm that the power of each resistor adds to the total power:

$$P_A + P_B = P_{tot} = \Delta V \cdot I_{tot}$$

$$\frac{(\Delta V)^2}{R} + \frac{(\Delta V)^2}{R} = \frac{2(\Delta V)^2}{R} = \frac{\Delta V}{1} \cdot \frac{2(\Delta V)}{R}$$

Part I: Solving Full Circuits Algebraically

I.4 ANSWER

a)

	Resistor A	Resistor B	Resistor C	Total (Battery)
Potential Difference	ΔV	ΔV	ΔV	ΔV
Current	$\frac{\Delta V}{R}$	$\frac{\Delta V}{R}$	$\frac{\Delta V}{R}$	$\frac{3(\Delta V)}{R}$
Resistance	R	R	R	$\frac{R}{3}$
Power	$\frac{(\Delta V)^2}{R}$	$\frac{(\Delta V)^2}{R}$	$\frac{(\Delta V)^2}{R}$	$\frac{3(\Delta V)^2}{R}$

b)

Confirm that the power of each resistor adds to the total power:

$$P_A + P_B + P_C = P_{tot} = \Delta V \cdot I_{tot}$$

$$\frac{(\Delta V)^2}{R} + \frac{(\Delta V)^2}{R} + \frac{(\Delta V)^2}{R} = \frac{3(\Delta V)^2}{R} = \frac{\Delta V}{1} \cdot \frac{3(\Delta V)}{R}$$