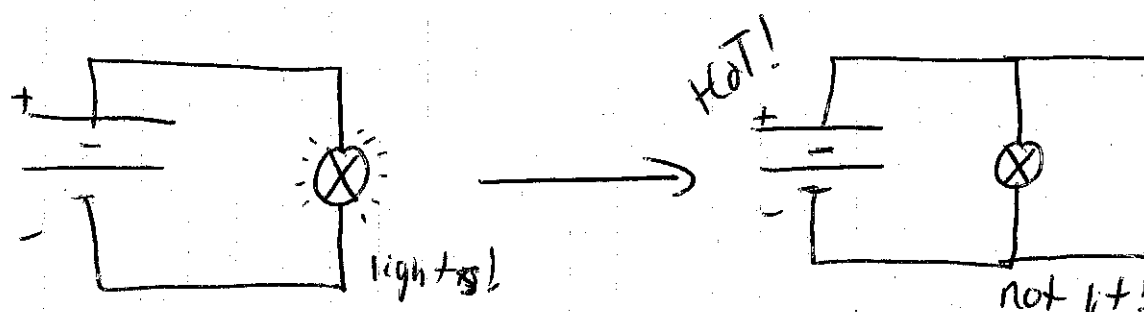


①


In previous pods, we saw that an extra wire can cause a light bulb to shut off and a battery to overheat.



In this pod, we will quantitatively analyze this situation.

In order to properly complete this, we need the following information:

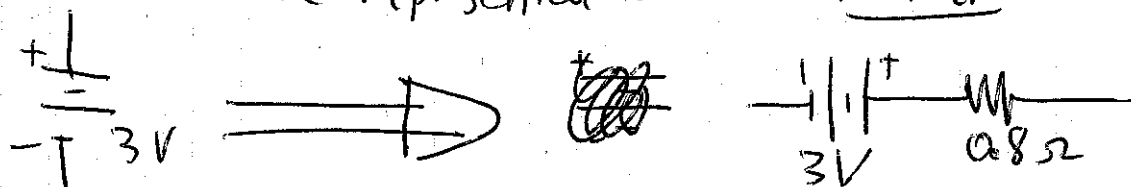- a tiny light bulb has a resistance of about 8 Ohms [light bulbs are actually non-ohmic resistors, but for this assignment we will pretend they are]
- Two AA batteries have an internal resistance of about 0.8 Ohms. This means, the battery should be represented with a resistor →




~~the~~

page 2


- we will assume that a small length of wire has a resistance of about  $0.01 \Omega$ .

~~then~~ Including all this information,  
~~our~~ our circuits will look like this.

~~correct circuit~~

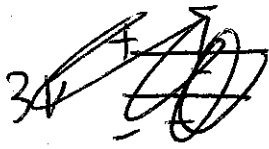


short circuit

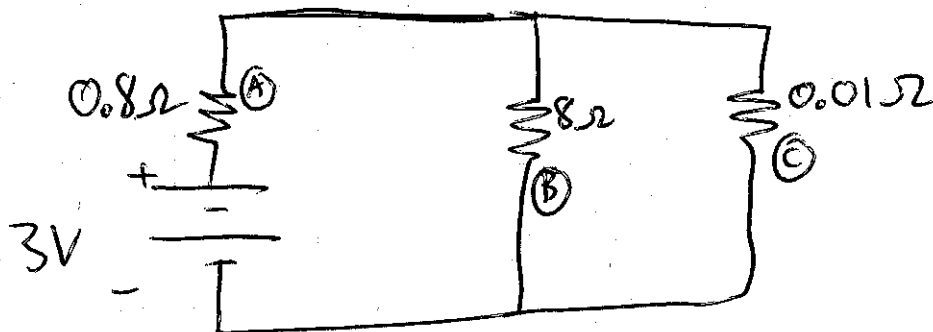

- Resistor (A) is the internal resistance of the battery, any power dissipated by resistor (A) will be heat dissipated by the battery.
- Resistor (B) represents the light bulb, any power dissipated by resistor (B) will be heat + light emitting from the bulb.

① Consider ~~the~~ the correctly constructed circuit below:

page 3

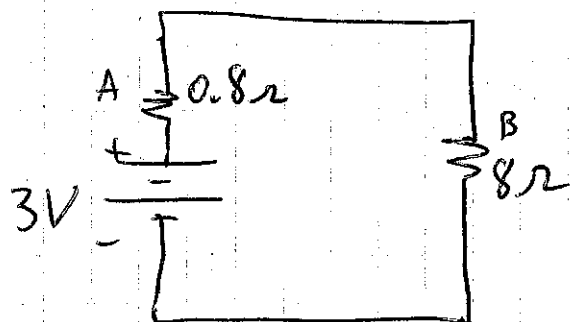

A - internal resistance of battery

B - light bulb

~~② Solve the incorrectly constructed circuit!~~


~~Find the~~

What is the power ~~is~~ dissipated by the internal resistance of the battery ①?

What is the power dissipated by the light bulb ②?

② Consider the incorrectly constructed circuit below

page  
4

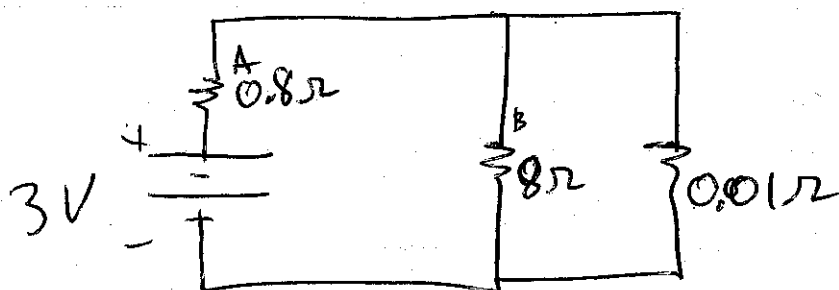

What is the power dissipated  
by the internal resistance of  
the battery (A)?

What is the power dissipated  
by the light bulb (B)?

- ③ The power of resistor A represents heat dissipated by the battery
- Did this value increase or decrease when the extra wire was added?
  - By what factor did it change?

- ④ The power of resistor B represents the brightness of the light bulb
- Did this value increase or decrease when the extra wire was added?
  - By what factor did it change?

- ⑤ We observe that, in real life, the extra wire makes the light bulb shut off, and the battery overheat

~~Is this~~ A

Is this quantitative analysis consistent with our observations?